

Tech & Teach

Digital Chip Design Program

RTL Design

Mohammed alkhalifah

Mohammedalnaif

Task #01

6/7/2026


Gate-level

Tech & Teach

Task #1.1

```
module t1(x1,x2,x3,f);  
  input x1,x2,x3;  
  output f;  
  wire [2:0]w;  
  
  and (w[0],x1,x2);  
  not(w[1],x2);  
  and (w[2],x3,w[1]);  
  or (f,w[0],w[2]);  
endmodule
```

Task #1.2

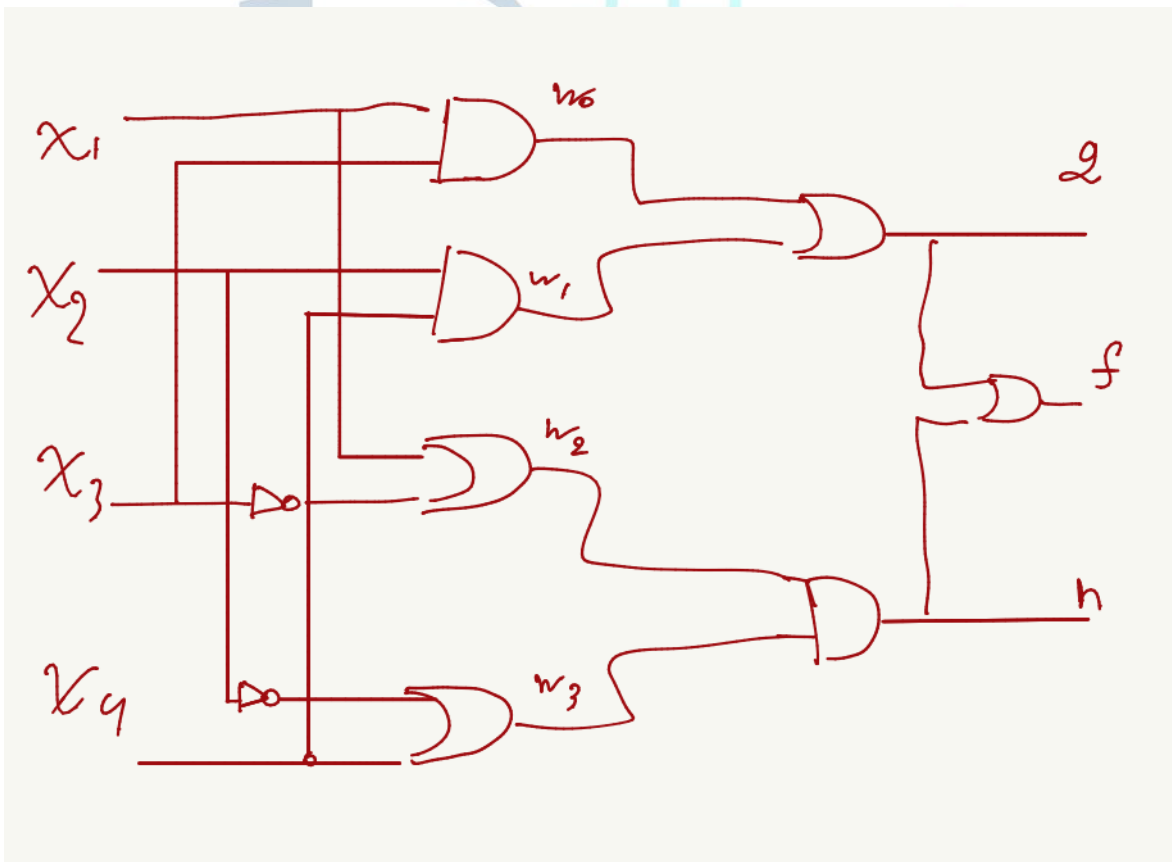

Task #1.3

```
module t1(AeqB, AltB, AgtB, a, b);
```

```
input [3:0] a,b;
```

```
output AeqB, AltB, AgtB;
```

```
wire [3:0]i, w;
```

```
xnor (i[0], a[0], b[0]);
```

```
xnor (i[1], a[1], b[1]);
```

```
xnor (i[2], a[2], b[2]);
```

```
xnor (i[3], a[3], b[3]);
```

```
and (AeqB, i[0], i[1], i[2], i[3]);
```

```
and (w[0], a[3], ~b[3]);
```

```
and (w[1], a[2], ~b[2], i[3]);
```


```
and (w[2], a[1], ~b[1], i[3], i[2]);
```

```
and (w[3], a[0], ~b[0], i[3], i[2], i[1]);
```

```
or (AgtB, w[0], w[1], w[2], w[3]);
```

```
nor (AltB, AgtB, AeqB);
```


```
endmodule
```

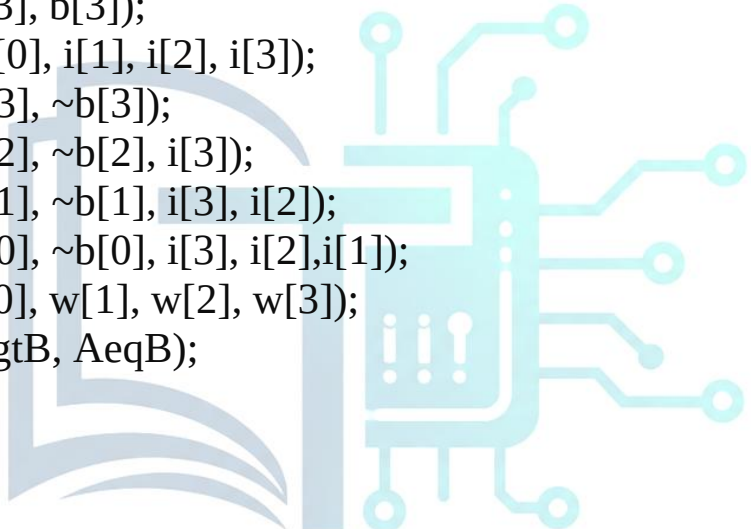

Tech & Teach

Work distribution

Section	Abdulmalek	Omar	Khaled
Report	✓		
Task n.x		✓	
Task n.x+1			✓

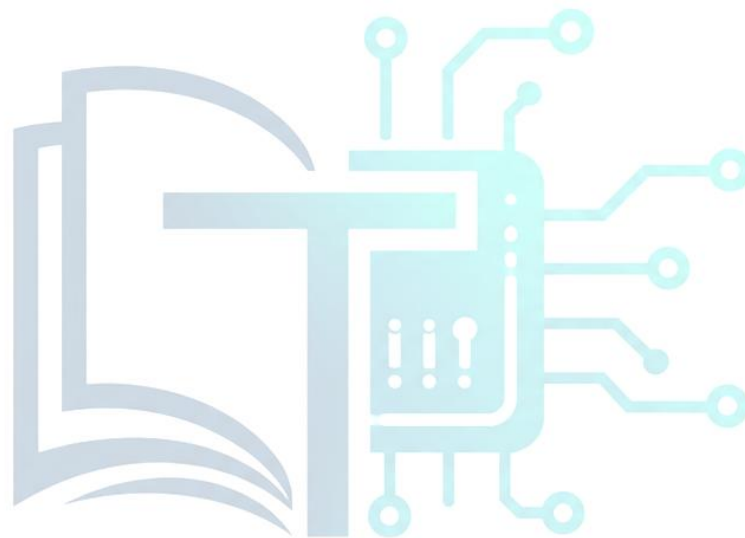

Tech & Teach